

--- University of Minnesota ---
Institute of Technology
Department of Electrical Engineering

Home Work #1
Due: Monday, October 5, 1998

EE5505: Analog Integrated Circuit Design

Fall 1998

- 1) Do problem 1.4
- 2) Do problem 1.5
- 3) Do problem 1.10
- 4) Do problem 1.11
- 5) Use HSPICE and MWAVES to plot the AC characteristics of the following circuit. Measure the small-signal gain at DC and also measure the unity gain frequency. The models for the MOS devices can be obtained from the web page set up for this class.

