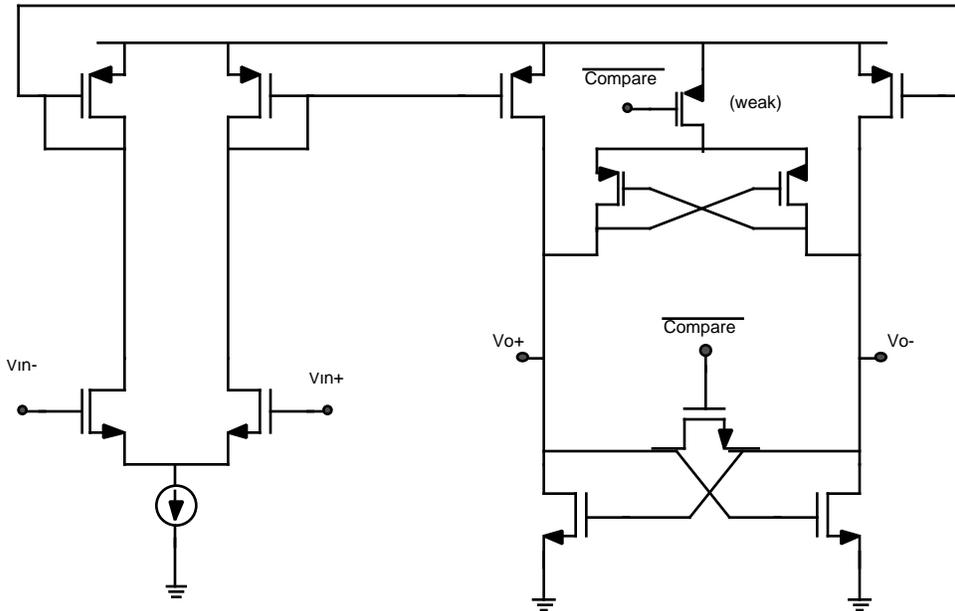


EE8331: Advanced Analog Integrated Circuit Design


HW #3
Due Monday 04/17/00

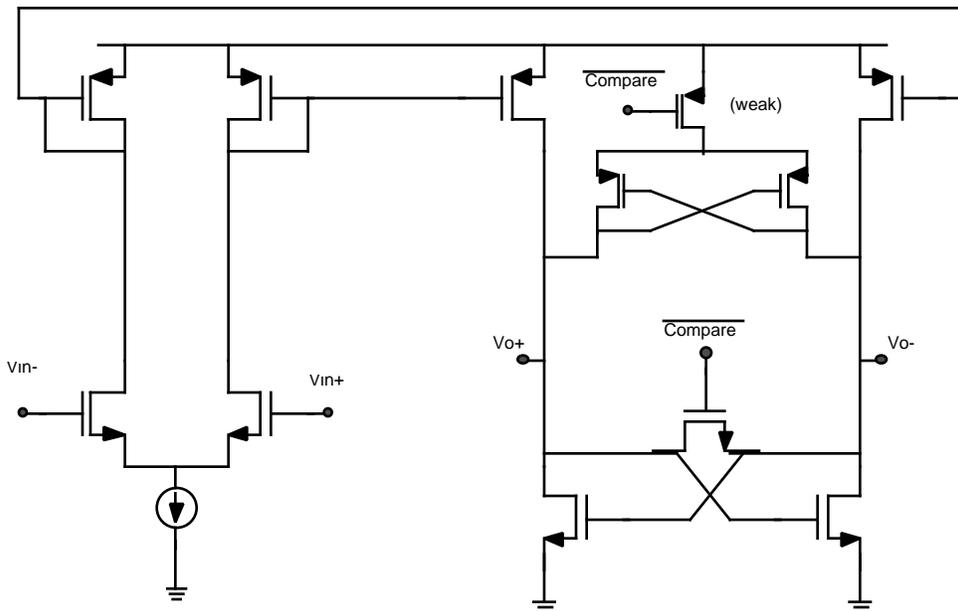
- 1) Develop an autozero scheme for the comparator shown below. Illustrate the result with a 10 mV input referred offset error and correcting it. Use simulation (SPICE) to illustrate this answer.

Comparator without flashback compensation or pull up scheme



Comparator with pull-up scheme but no flashback compensation



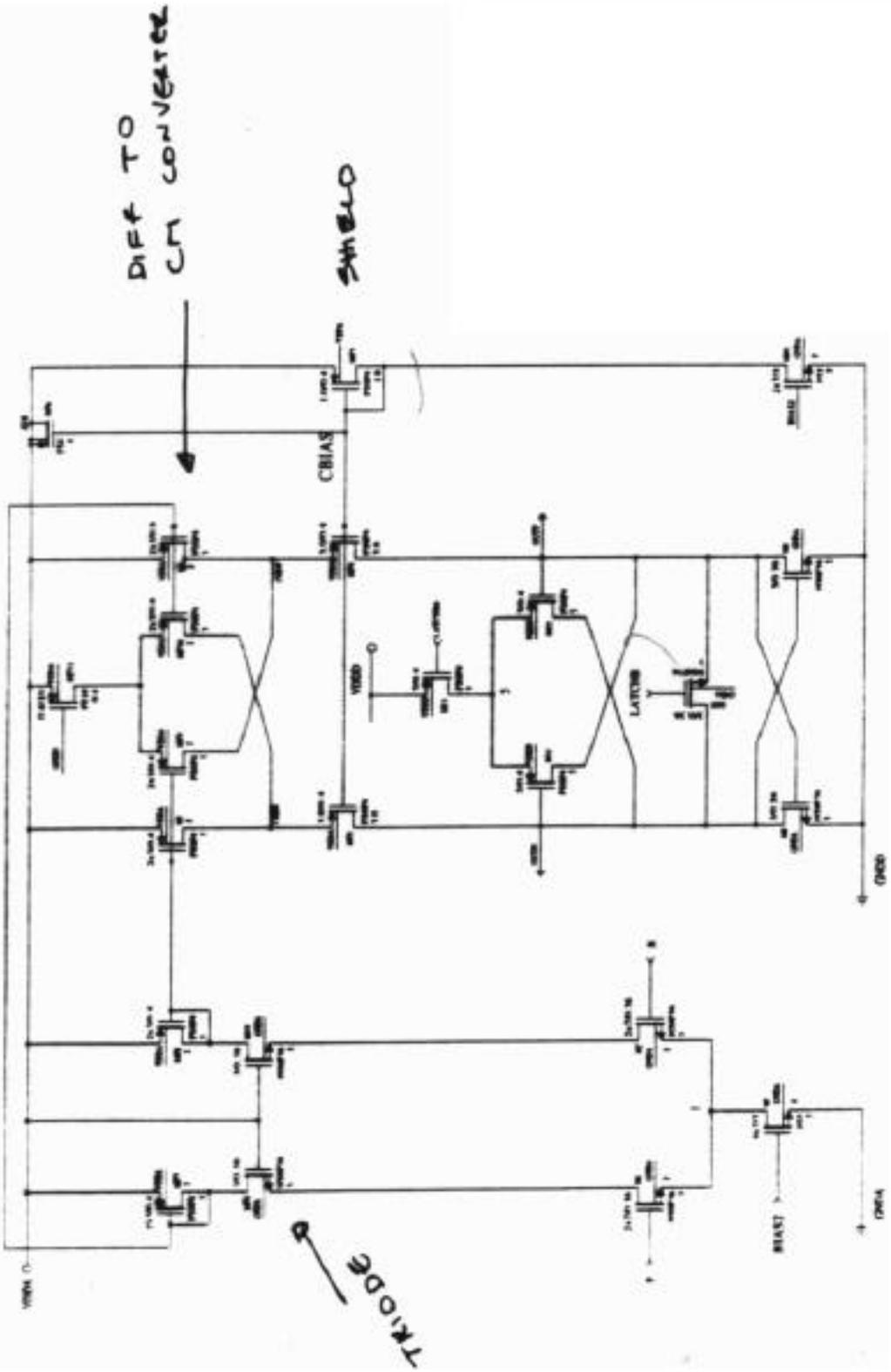

DIFF TO
CM CONVERTER

SHIELD

TRIODE

BIAS

LATCHING

VDD1

VDD2

VDD3

VDD100